

DIGITAL SYSTEM DESIGN



Building Block Circuits

- Rather than building systems at the gate level, often digital systems are constructed from higher level, but still basic, building block circuits.
- Multiplexers, decoders, flip-flops, registers, and counters are examples of building blocks, which are subcircuits from which complex circuits can be constructed.
- For many larger systems, the circuitry required can often be divided into two Sub-systems: the **datapath circuit; and the control circuit**.
- The *datapath* circuit is used to store and manipulate data and to transfer data from one part of the system to another.
- Datapath circuits can comprise of building blocks such as registers, shift registers, counters, multiplexers, decoders, etc.


Building Block Circuits

- The *control* circuit, usually an FSM, controls the operation of the datapath circuit.
- In many applications, it is useful to be able to prevent the data stored in a flip-flop from changing when an active clock edge occurs.
- A simple example of the division of the data path and the control path can be illustrated using a flip-flop with an enable input.
- The data path consists of the flip-flop and its input, and the control path consists of the enable input.
- The two paths exist independently of each other with the enable (control path) controlling the flow of the data into the flip-flop.
- It is also useful to be able to inhibit the shifting operation in a shift register by using an enable input.


Algorithmic State Machine (ASM) charts

- State diagrams are not convenient to describe the behavior of large state machines
- ASM charts are used to describe large machines
 - ▣ It is a type of flow chart
 - ▣ Represents state transitions
 - ▣ Represent generated outputs for an ASM
- ASM charts have three types of elements
 - ▣ State box
 - ▣ Decision box
 - ▣ Conditional output box


Elements used in ASM charts

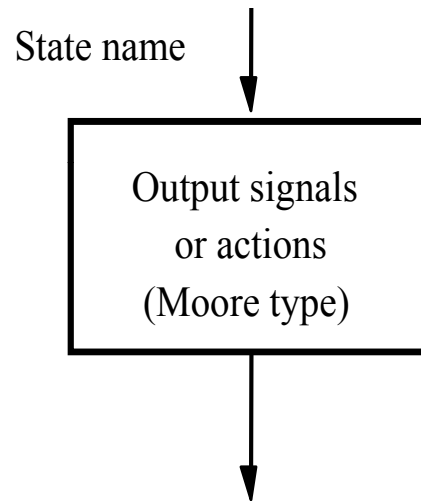


(a) State box

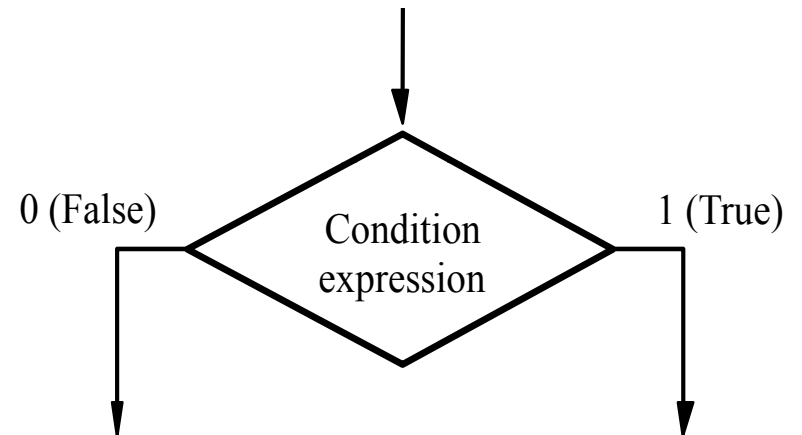



(b) Decision box

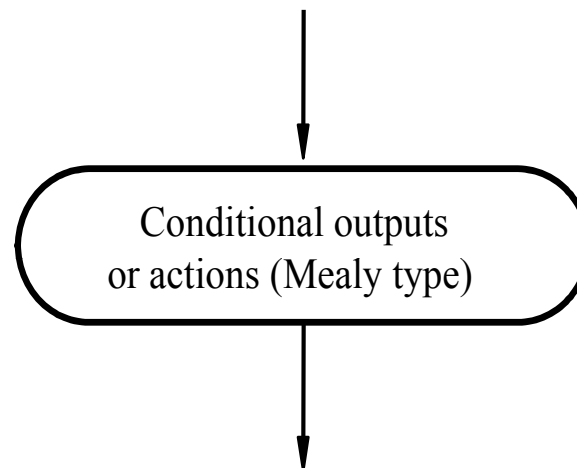

ASM chart for a simple FSM

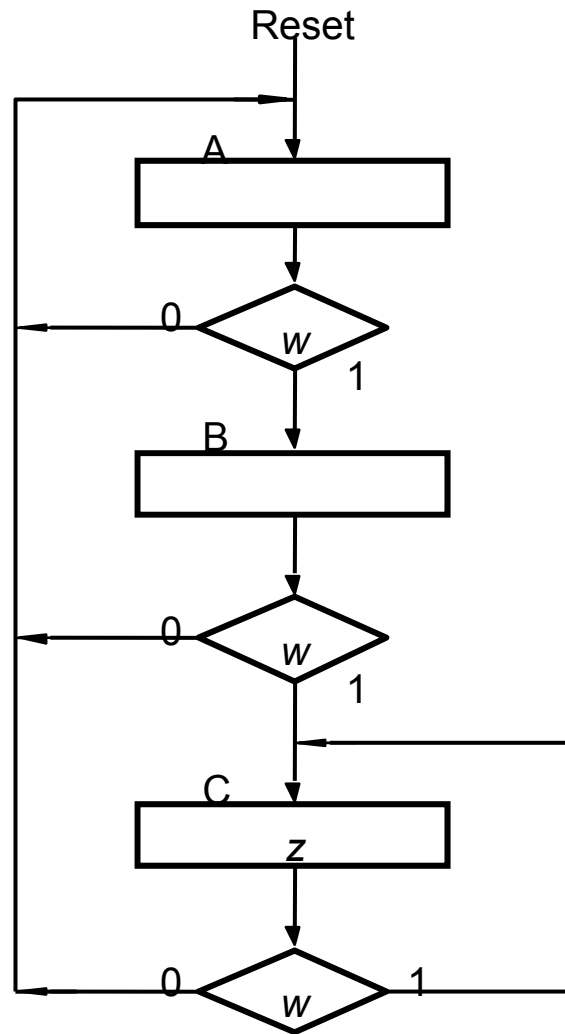

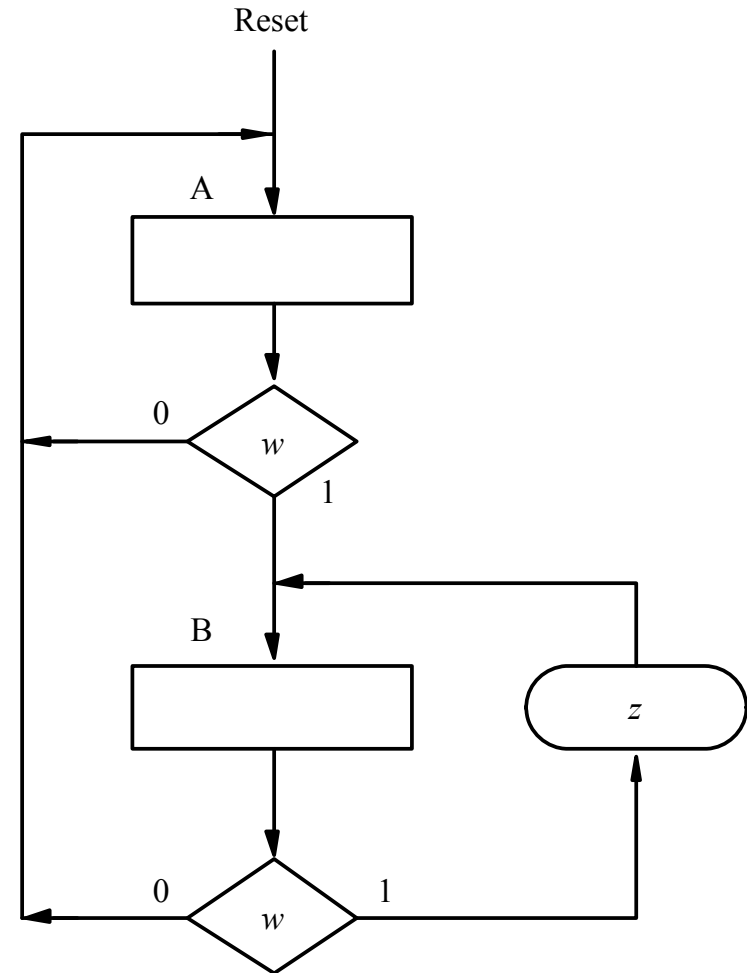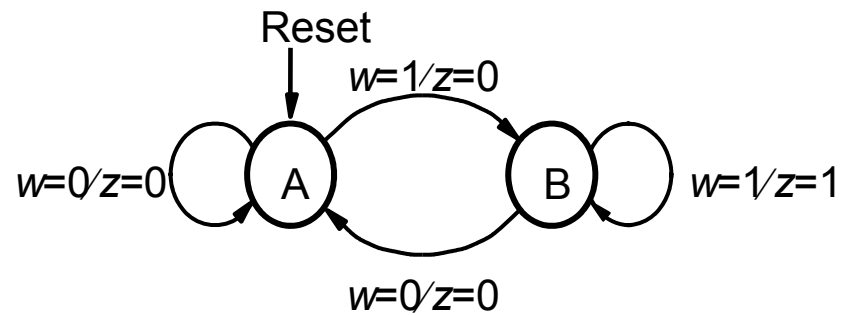State Diagram and its corresponding ASM chart




Design Example: A Bit-Counting Circuit

- Using the concepts of the ASM and the separate data and control circuits we can implement fairly complex systems.
- Suppose we wish to count the number of bits in a register that have the value 1.
- Assume that the value A is stored in a register that can shift its contents in the left to-right direction.
- Pseudo-code for the bit counter.

```
B=0;
while A ≠ 0 do
    if  $a_0 = 1$  then
        B=B+1;
    End if;
    Right-shift A ;
End while;
```



ASM chart for the pseudo-code.

- s: input signal that indicates if A has been loaded
- We can assume that the same clock signal controls the changes in the state of the machine and changes in A and B. Therefore in state S2, the decision box which tests whether $A=0$, occurs simultaneously with the box that checks the value of a_0 .
- If $A=0$, then the FSM will change to state S3 on the next clock edge (this also shifts A, which has no effect because A is already 0).
- On the other hand, if $A \neq 0$, then the FSM does not change to S3 but remains in S2. At the same time A is shifted, and B is incremented if a_0 has the value 1.

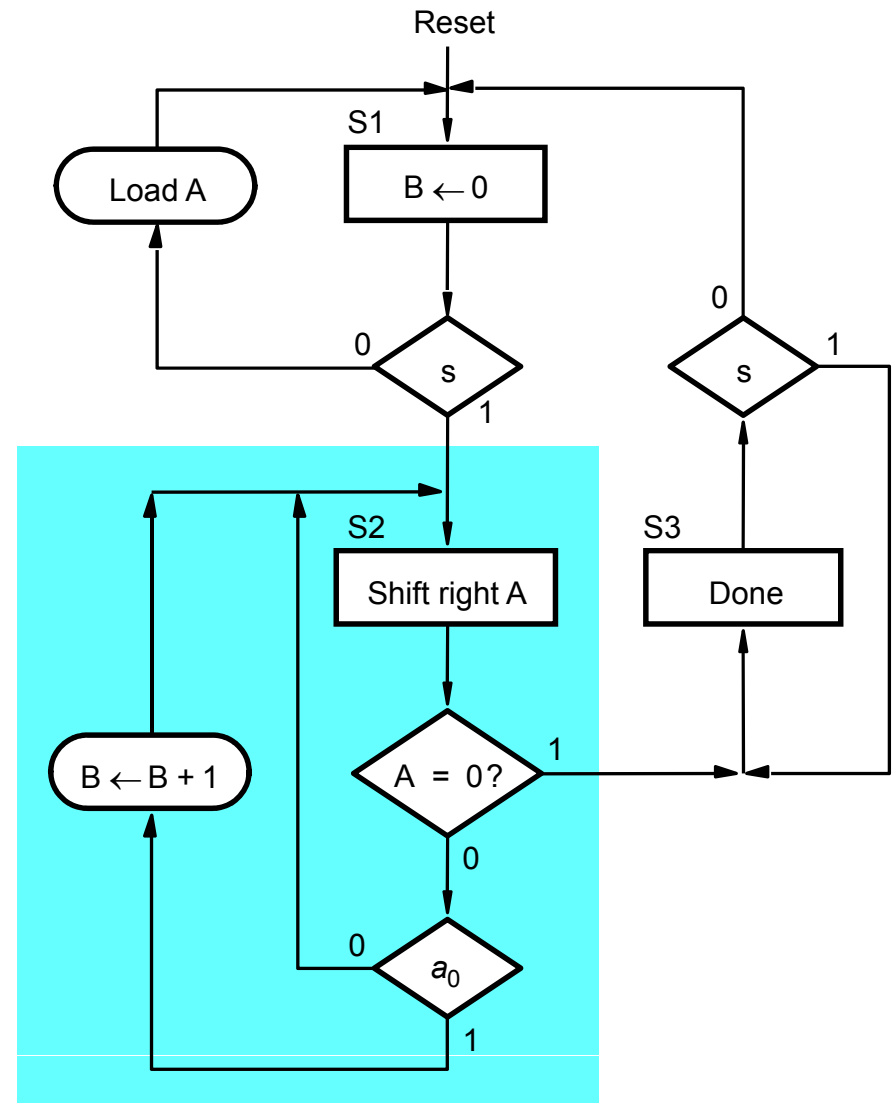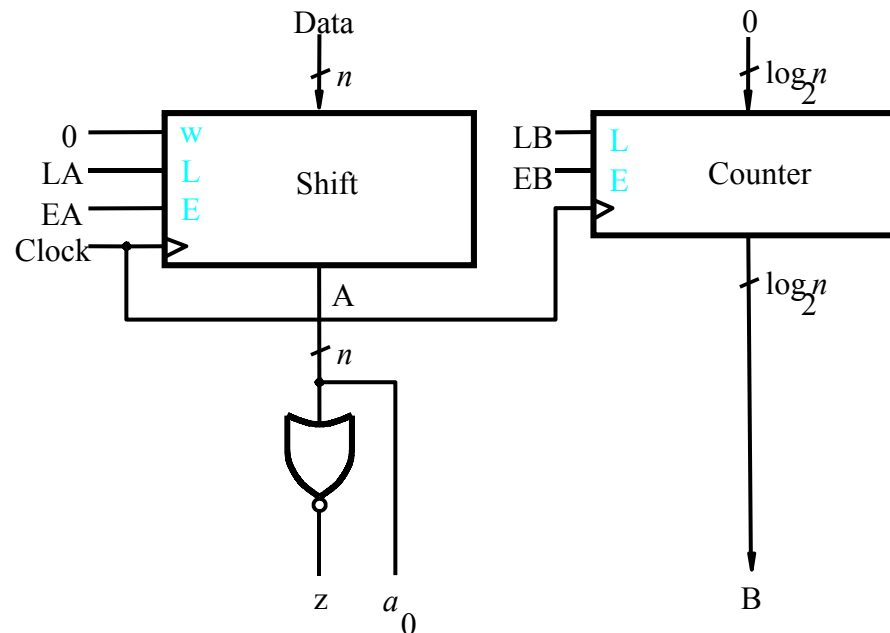


A Bit-Counting Circuit (data-path)

- For the data-path circuit a shift register which shifts left to-
- right is required to implement A.
- It must have the parallel load capability and an enable input since shifting should occur only in state S2.
- In addition, a counter is needed for B, and it needs a parallel-load capability to initialize the count to 0 in state S1.



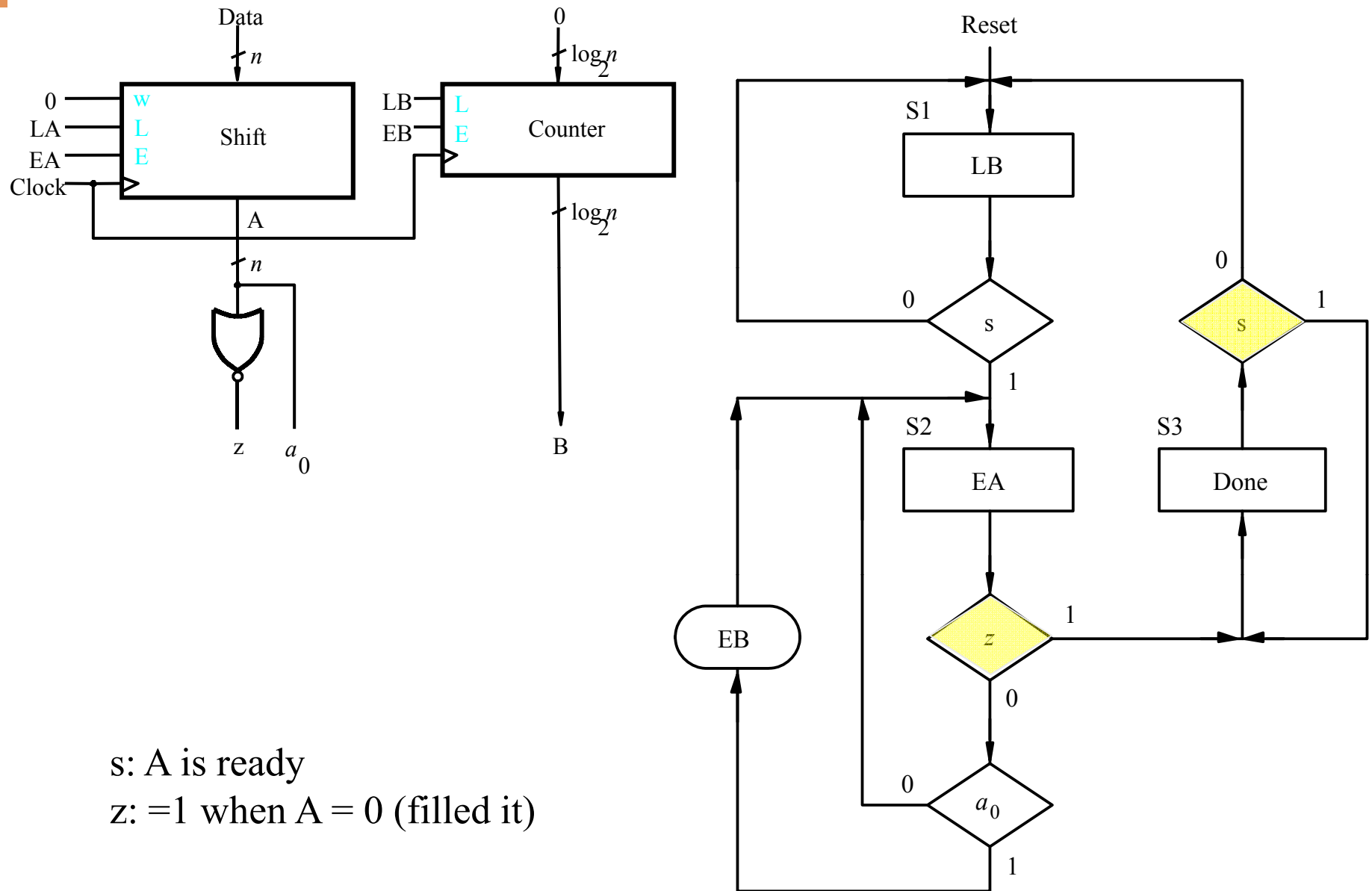
ASM chart for the bit counter control circuit



s: A is ready

z: =1 when A = 0 (filled it)

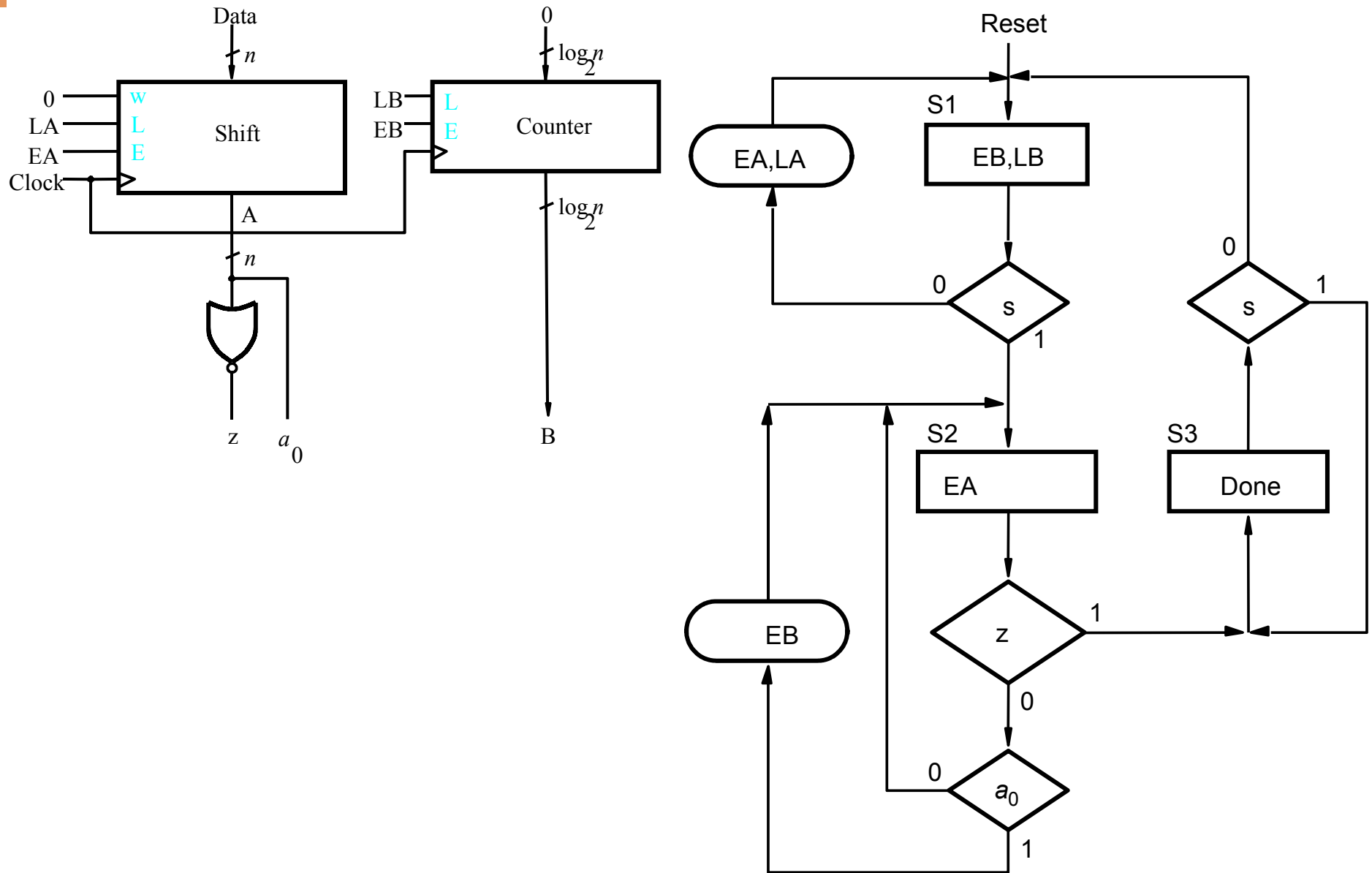ASM chart for the bit counter control circuit



Shift-And-Add Multiplier

Decimal	Binary	
13	1 1 0 1	A: Multiplicand
$\times 11$	$\times 1 0 1 1$	B: Multiplier
13	1 1 0 1	
13	1 1 0 1	
143	0 0 0 0	
	1 1 0 1	
	1 0 0 0 1 1 1 1	P = Product

Note: In the original image, blue arrows indicate the shifting of the multiplicand (1101) to the left by 0, 1, 2, and 3 positions, which are then added to form the final product 10001111.

Manual method


An algorithm for multiplication.

```


P = 0 ;
for i = 0 to n - 1 do
    if  $b_i = 1$  then
         $P = P + A$  ;
    end if;
    Left-shift A ;
end for;
    
```

ASM chart for the multiplier

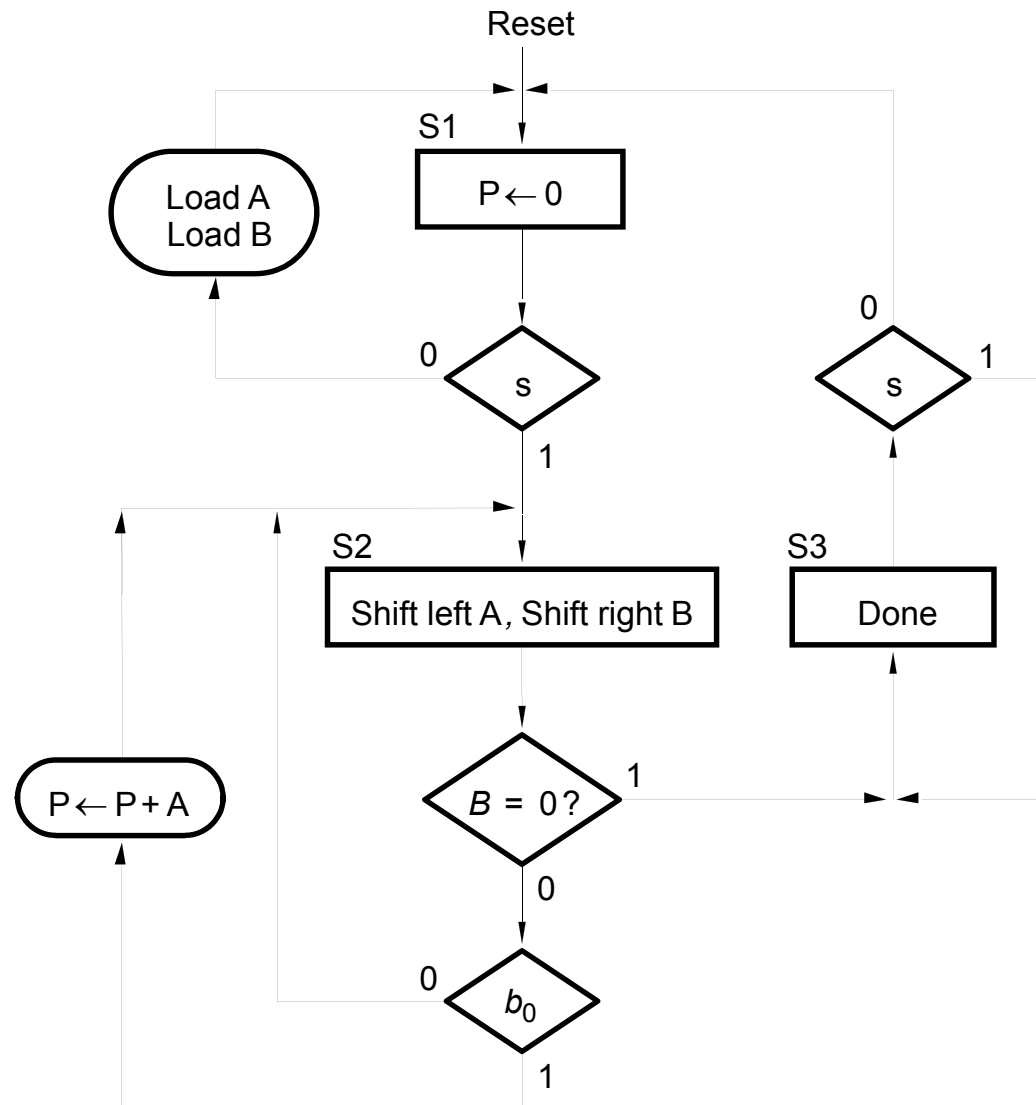$P = 0$;
for $i = 0$ to $n - 1$ do
 if $b_i = 1$ then
 $P = P + A$;
 end if;
 Left-shift A ;
end for;



Datapath circuit for the multiplier.

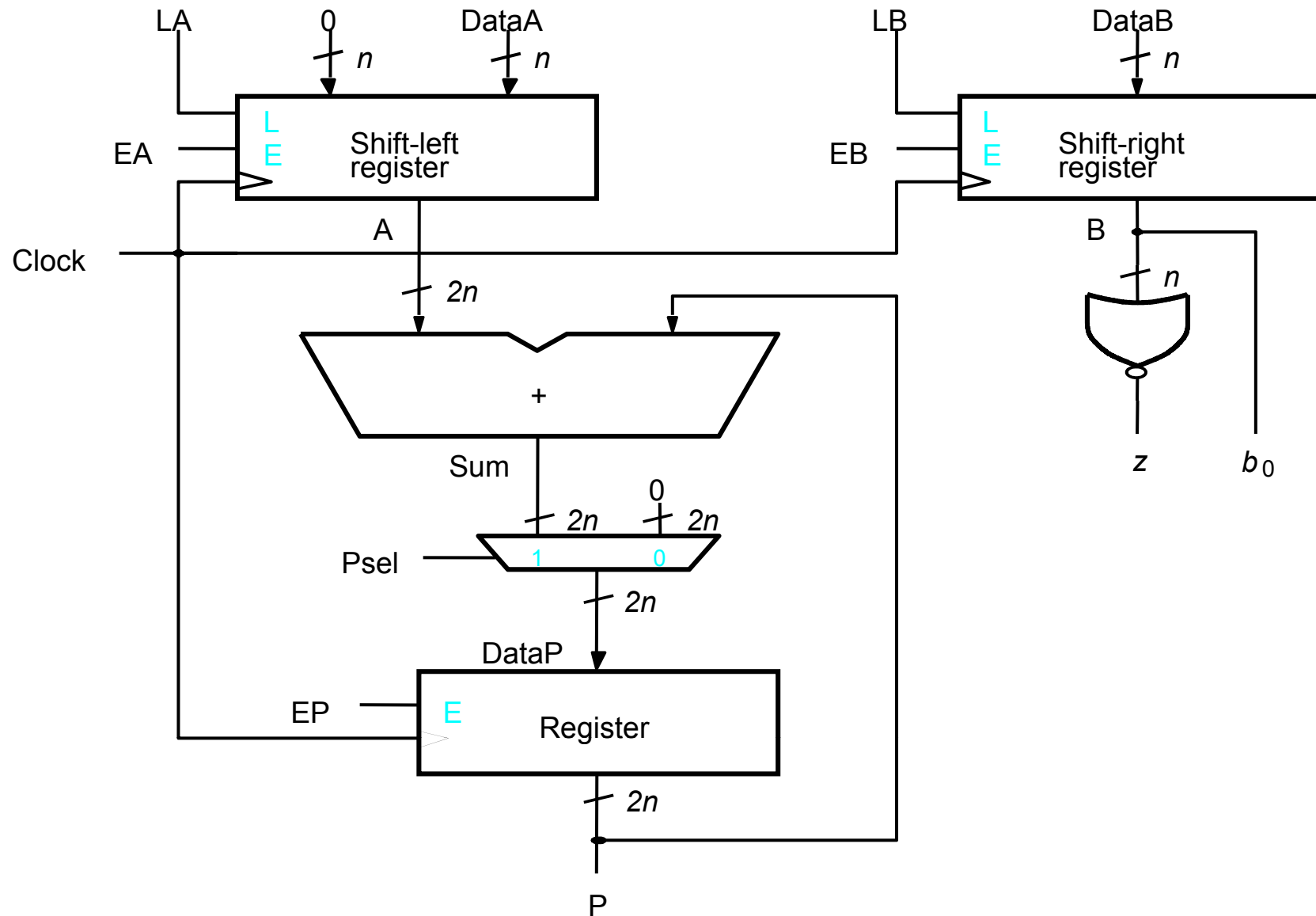

ASM chart for the multiplier control circuit.

